

Exploratory Questions

1. How does a voltmeter actually measure voltage across a component in a circuit?
2. What purpose does a Wire Wound resistor serve that a Carbon Film resistor cannot?
3. Although wires are considered to be perfect conductors in circuit analysis, what numerical impact do extremely long wires have on voltage drop in the real world?